

ECSE 281 HW

Tyler
Youk

1. Implement the following function using only
74x138 Binary decoder & NAND Gates


$$F = \prod_{ABC} (3, 4, 5, 6, 7)$$

$$F = \sum_{w,x,y,z} (2, 3, 4, 5, 8, 10, 12, 14)$$

74x138 Binary Decoder \rightarrow Active Low
& NAND gates

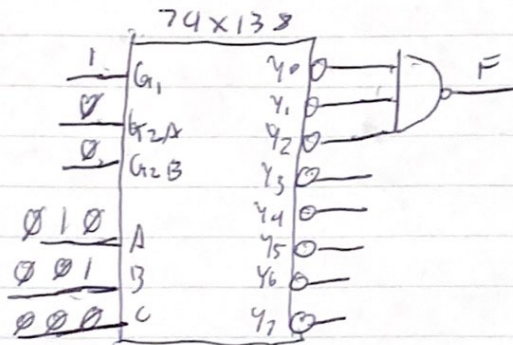
a. ~~XXXX~~

Maxterms: Offsets \rightarrow Product of Sums



$$F = \prod_{ABC} (3, 4, 5, 6, 7)$$

$$= F = \sum_{ABC} (1, 2, 3)$$

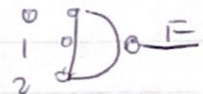


Active Low

NAND
F=1

AND
F=0

b. $F = \sum_{w,x,y,z} (2, 3, 4, 5, 8, 10, 12, 14)$

Sum of Products = Minterms
(Onsets)

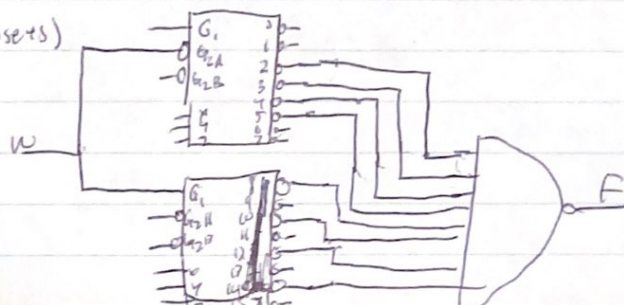

Tyler
Youk

2. Design a 10 to 4 encoder w/ the inputs 1 on ut 10 code
 & output coded ~~more~~ normally for 0-7 [binary 0000-0111]
 & 8 coded as E [1110]
 & 9 coded as F [1111]

Show the internal circuit


10 to 4 encoder

$$Y_3: I_8 + I_9$$

$$Y_2: I_4 + I_5 + I_6 + I_7 + I_8 + I_9$$


$$Y_1: I_2 + I_3 + I_6 + I_7 + I_8 + I_9$$

$$Y_0: I_1 + I_3 + I_5 + I_7 + I_9$$

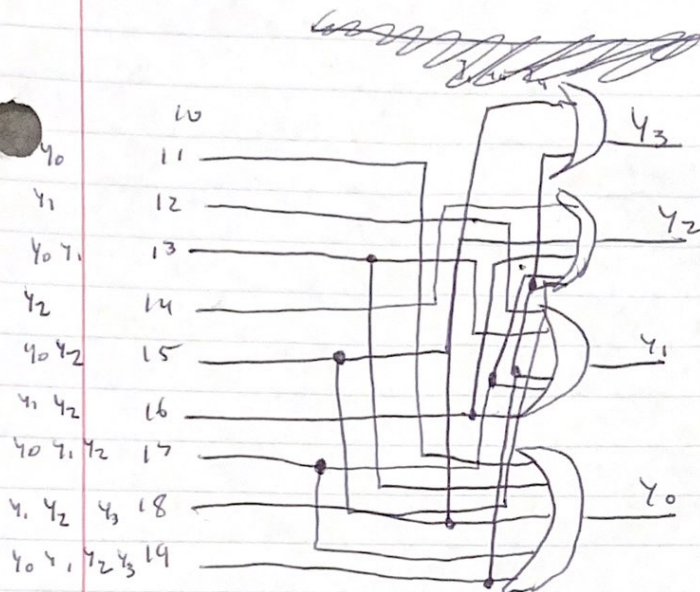

3. Implement the following only using a single 4x1 multiplexer & inverters

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

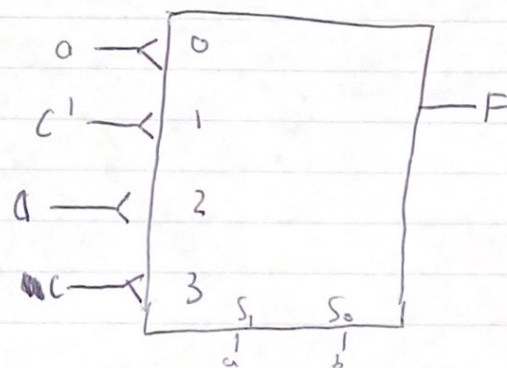

type-700K

9. For the logic expression below, find all of the static hazards and design a hazard-free circuit that realizes the same logic function.

~~$F = w \cdot x$~~

$$F = w \cdot x + w' \cdot y'$$

$$F = w \cdot y + w' \cdot z' + x \cdot y' \cdot z$$

		y			
y	w _x	00	01	11	10
	0	0	1	1	
	1	1	1	1	

Static hazard $x \cdot y'$

$w' \cdot y'$

$w \cdot x$

$$F = w' \cdot y' + w \cdot x + x \cdot y'$$

$x \cdot w' \cdot y' \text{ hazard}$

		w			
y _z	w _x	00	01	11	10
	00	1	1		
	01		1	1	
	11			1	1
	10	1	1	1	1

$w' \cdot z'$

x

$w \cdot y$

$w \cdot x \cdot y \text{ hazard}$

$x \cdot y' \cdot z$

$y \cdot z' \text{ hazard}$

$w \cdot y + w' \cdot z' + x \cdot y' \cdot z$

$$F = \underbrace{w \cdot y + w' \cdot z' + x \cdot y' \cdot z}_{\text{original}} + \underbrace{x \cdot w' \cdot y' + y \cdot z' + w \cdot x \cdot y}_{\text{hazards}}$$

Tyler York

5. Design an 8×1 multiplexer (8 data sources/ 1 bit data from each source)

using 2×1 multiplexers only. You can use as many 2×1 multiplexers as needed. Clearly label all inputs and outputs.

8 inputs

